

**AQA, Edexcel**

**A Level**

# A Level Physics

## Capacitors

Name:

**M M E**

Mathsmadeeasy.co.uk

Total Marks: /30

1. George wishes to explore the rules for multiple capacitors. To do this, he constructs a circuit using three:  $C_1$  is connected in series with  $C_2$ ; these are both connected in parallel with  $C_3$ . All are connected to a 6 V power supply.  $C_1 = 10 \mu F$ ,  $C_2 = 20 \mu F$  and  $C_3 = 50 \mu F$ .

Total for Question 1: 13

- (a) Explain in terms of the flow of electrons how a potential difference is built up across a capacitor. [3]

- (b) Which of the following is correct? For two capacitors in series, irrespective of their capacitances, the charge stored by the first will be... [1]
- Half of that stored by the second.
  - The same as that stored by the second.
  - Twice that stored by the second.

- (c) In any circuit, charge is conserved. Use this, in combination with Kirchoff's laws, to show that the total capacitance of two capacitors in series is given by  $\frac{1}{C_{total}} = \frac{1}{C_1} + \frac{1}{C_2}$ . [3]

(d) Using similar techniques, it can be shown that  $C_{total} = C_1 + C_2$ . For George's circuit, calculate the following:

i. The total capacitance of the circuit.

[3]

ii. The reading on a voltmeter placed across capacitor 1.

[3]

2.

Total for Question 2: 6

(a) What is represented by the area underneath a graph of the potential difference across a resistor against the charge stored by it? [1]

(b) From the equation  $W = \frac{1}{2}QV$ , derive two other equations for the energy stored in capacitor. One should not include the term  $V$  and one should not include the term  $Q$ . [3]

(c) State the effect of each of the following on the energy stored by a capacitor. [2]

i. Doubling the potential difference across it.

ii. Halving the capacitance.

3. Ella charges a  $50\ \mu\text{F}$  capacitor using a  $6\ \text{V}$  power supply. She then discharges it through a resistor of resistance  $R$  (connected in parallel).

Total for Question 3: 11

- (a) Outline an experiment that Ella could perform to demonstrate the discharge characteristics of a capacitor when it is discharging through a resistor. Include a circuit diagram. [3]

- (b) After  $10\ \text{s}$ , the charge has reduced by  $99\ \mu\text{C}$  from its initial value of  $300\ \mu\text{C}$ . Calculate  $R$ . [2]

(c) Calculate the current in the circuit  $2\tau$  after the switch has been turned on.

[2]

(d) Once it has completely discharged, Ella recharges the capacitor using the same 6 V power supply.  
Calculate the potential difference across the capacitor after 5 s.

[2]

- (e) Sketch, on a single set of axes, the variation of  $V_C$ ,  $V_R$  and  $V_0$  with time during charging.  $V_C$ ,  $V_R$  and  $V_0$  are the potential differences across the capacitor, the resistor and the power supply respectively. [2]